

International
IR Rectifier

DESIGN TIPS

DT 04-4

International Rectifier • 233 Kansas Street, El Segundo, CA 90245 • USA

Using monolithic high voltage gate drivers

by

A. Merello, A. Rugginenti, M. Grasso

Design Tips

Using monolithic high voltage gate drivers

Table of contents

| | |
|--|-----------|
| INTRODUCTION | 1 |
| BOOTSTRAP CIRCUIT | 2 |
| <i>Bootstrap capacitor sizing</i> | 2 |
| <i>Considerations about bootstrap circuit</i> | 3 |
| GATE RESISTANCES | 4 |
| <i>Sizing the turn-on gate resistor</i> | 5 |
| Switching-time | 5 |
| Output voltage slope | 6 |
| <i>Sizing the turn-off gate resistor</i> | 6 |
| PARASITIC ELEMENT EFFECTS | 8 |
| <i>COM below Ground (Vss-COM)</i> | 8 |
| <i>V_S below Ground (Vss-Vs)</i> | 11 |
| Resistor between V _S and V _{out} | 11 |
| Clamping diode for V _S | 13 |
| PCB LAYOUT TIPS | 13 |
| <i>Distance from high to low voltage</i> | 13 |
| <i>Ground plane</i> | 13 |
| <i>Gate drive loops</i> | 13 |
| <i>Supply capacitors</i> | 14 |
| <i>Routing and placement example</i> | 14 |

INTRODUCTION

The purpose of this paper is to highlight the most common subjects driving a half bridge power stage in motor drive applications (with monolithic IC gate driver) and to suggest appropriate solutions to solve the issues.

In the following sections different topics are discussed: the sizing of some fundamental components, as bootstrap circuit and on/off gate resistors; the half bridge parasitic elements are presented with their effects and some possible solutions are proposed. In the end section some layout tips are presented.

All the situations and the solutions proposed are, where it's not specified, for a typical IR monolithic gate driver with floating bootstrap supply.

